

CS 61C: Great Ideas in Computer
Architecture (Machine Structures)
Single-Cycle CPU
Datapath & Control Part 2

Instructors:

Krste Asanovic & Vladimir Stojanovic
<http://inst.eecs.berkeley.edu/~cs61c/>

Review: Processor Design 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology

Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer


Step 2: Select set of datapath components & establish clock methodology

Step 3: Assemble datapath components that meet the requirements


Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

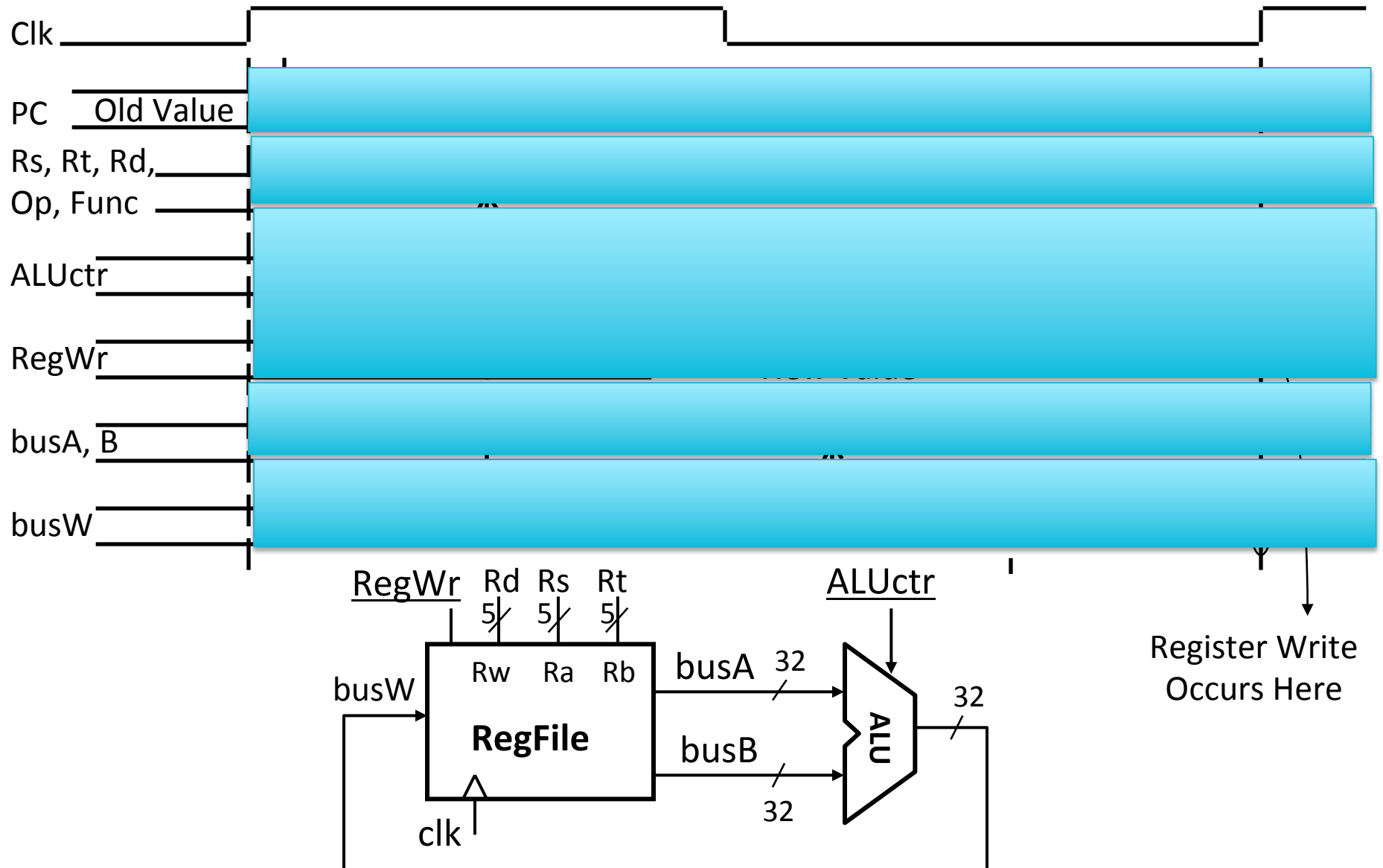Register-Register Timing: One Complete Cycle (Add/Sub)




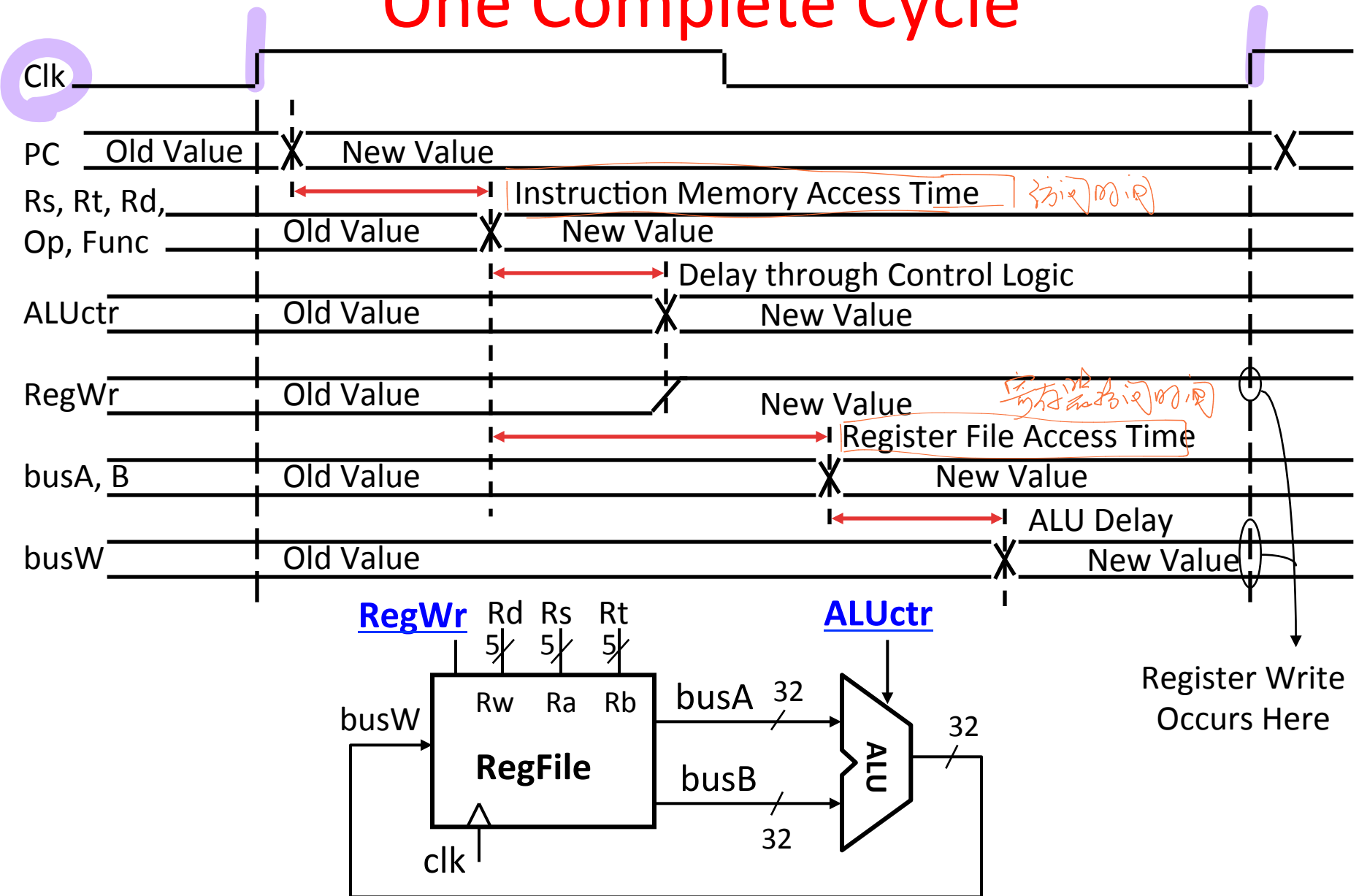Register-Register Timing: One Complete Cycle



3c: Logical Op (or) with Immediate

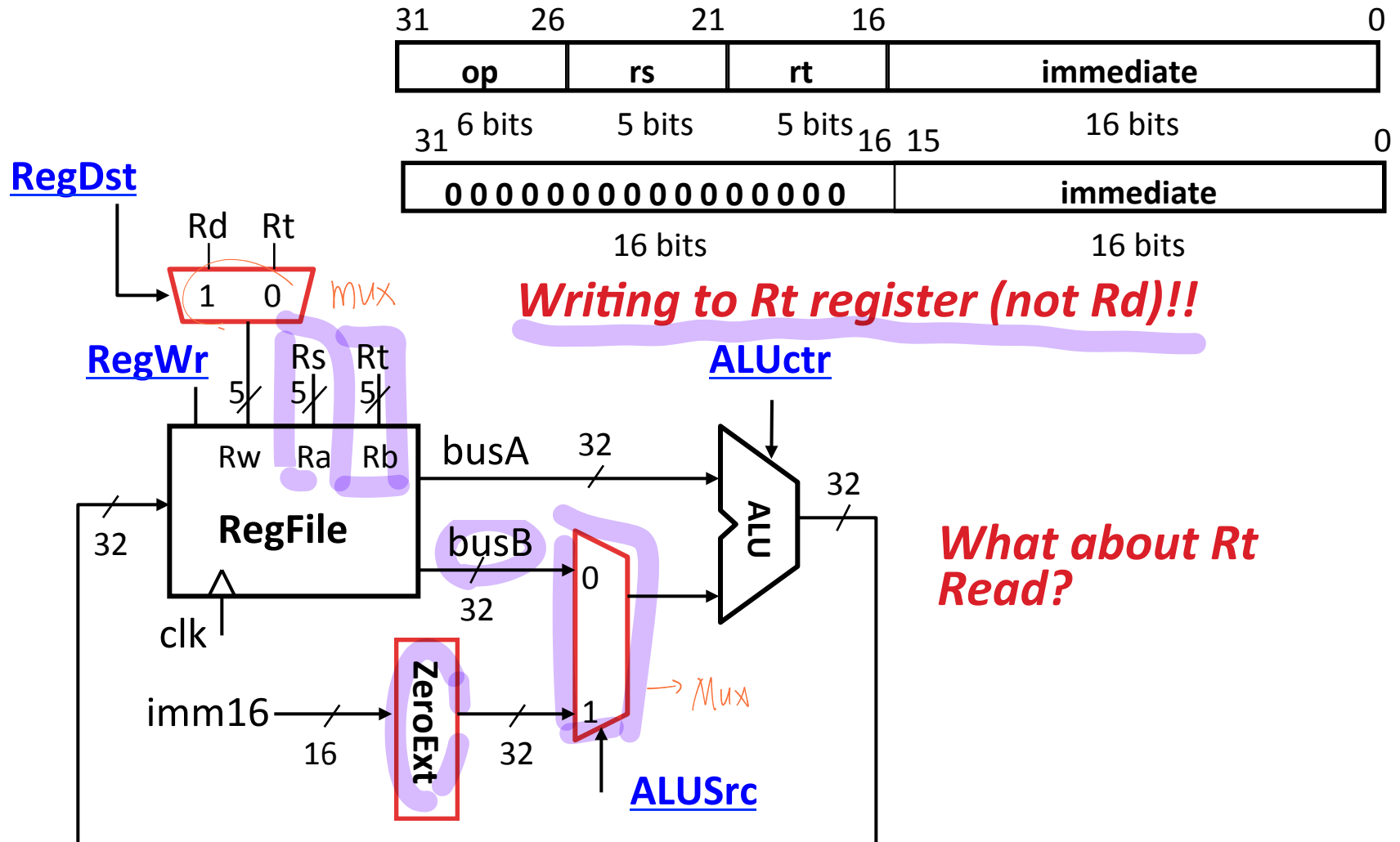
- $R[\text{rt}] = R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



3d: Load Operations

- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$


Example: `lw rt,rs,imm16`

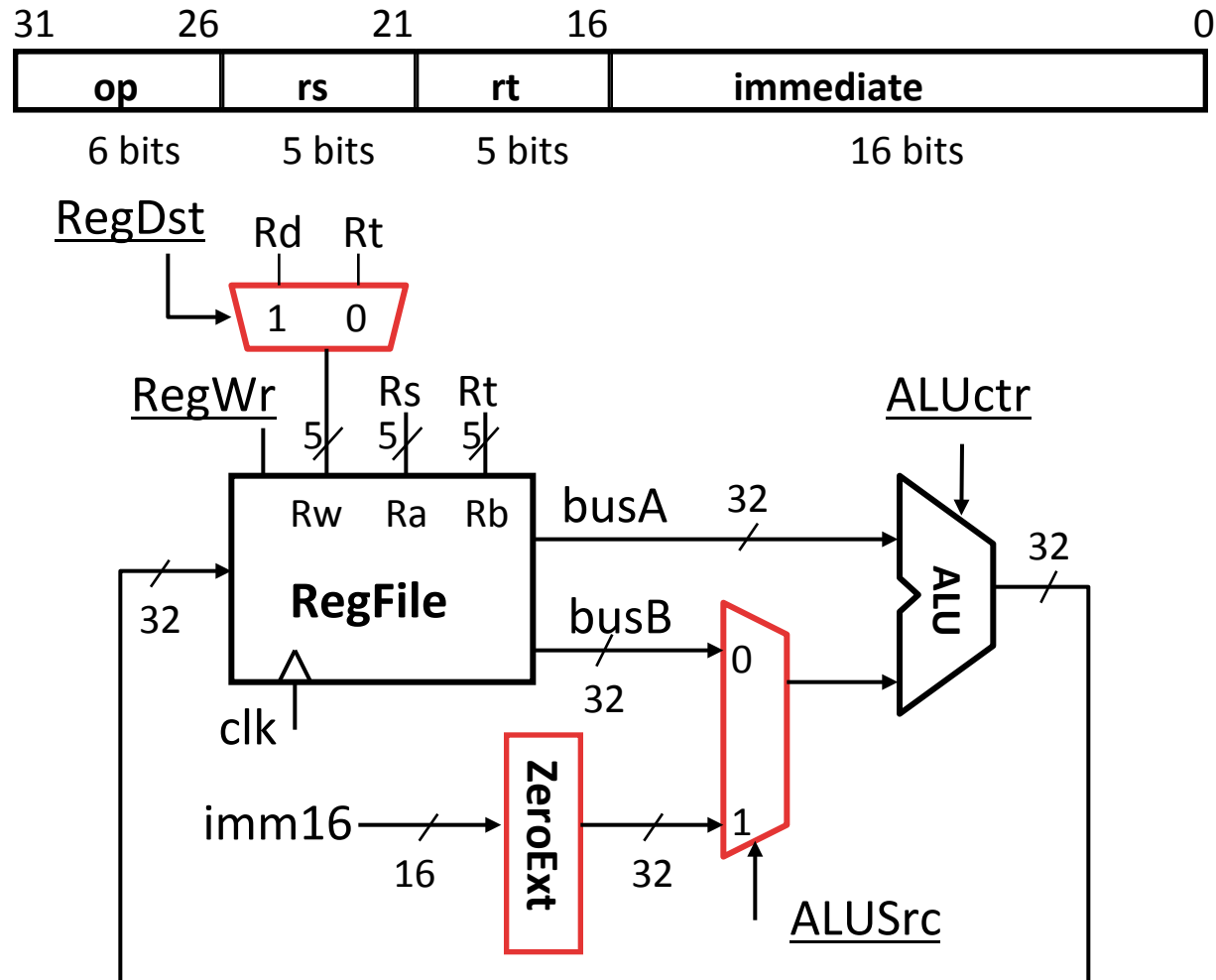

3d: Load Operations

- $R[\text{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$



Example: `lw rt, rs, imm16`

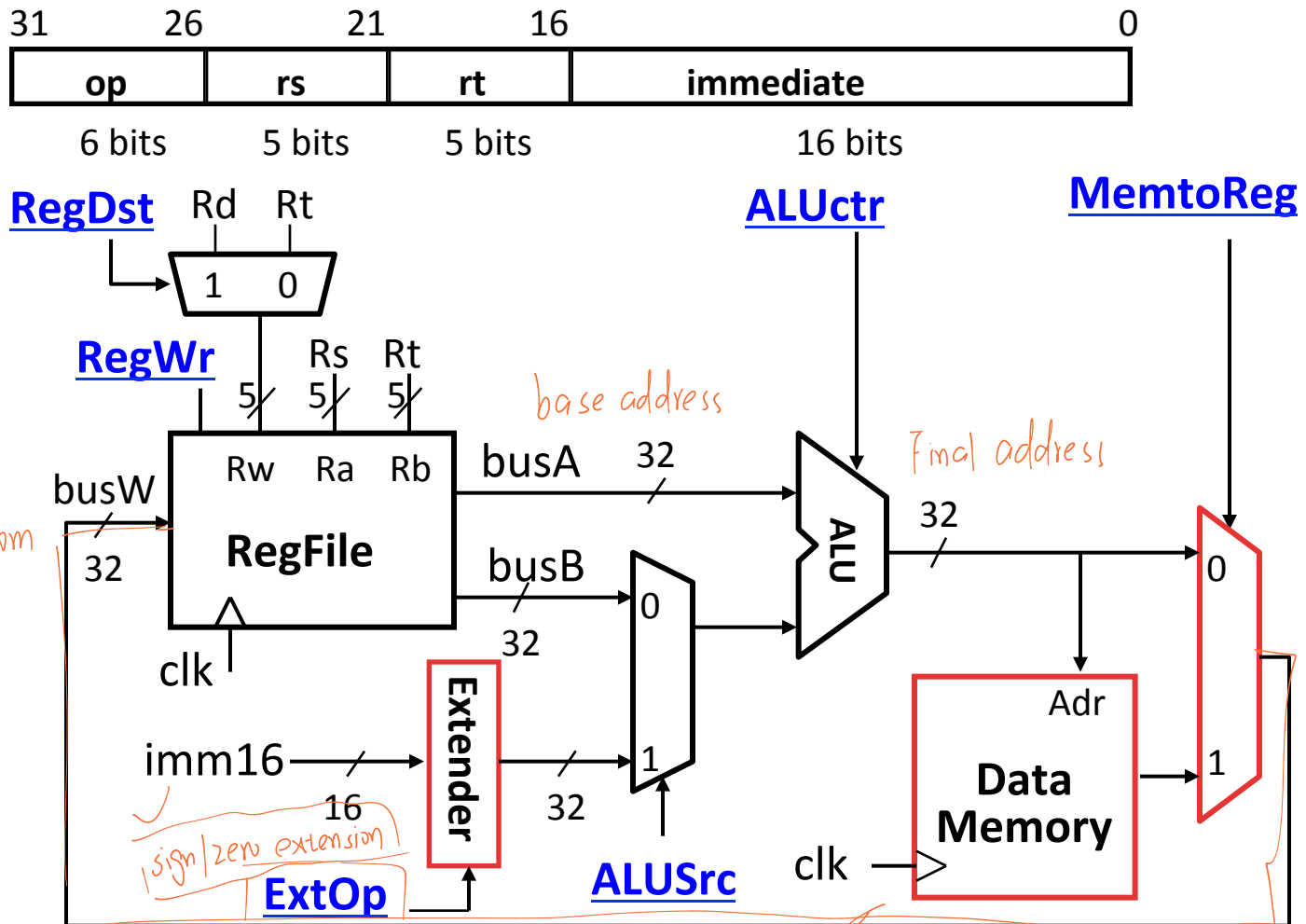

3e: Store Operations

- $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]] = R[\text{rt}]$



Ex.: `sw rt, rs, imm16`

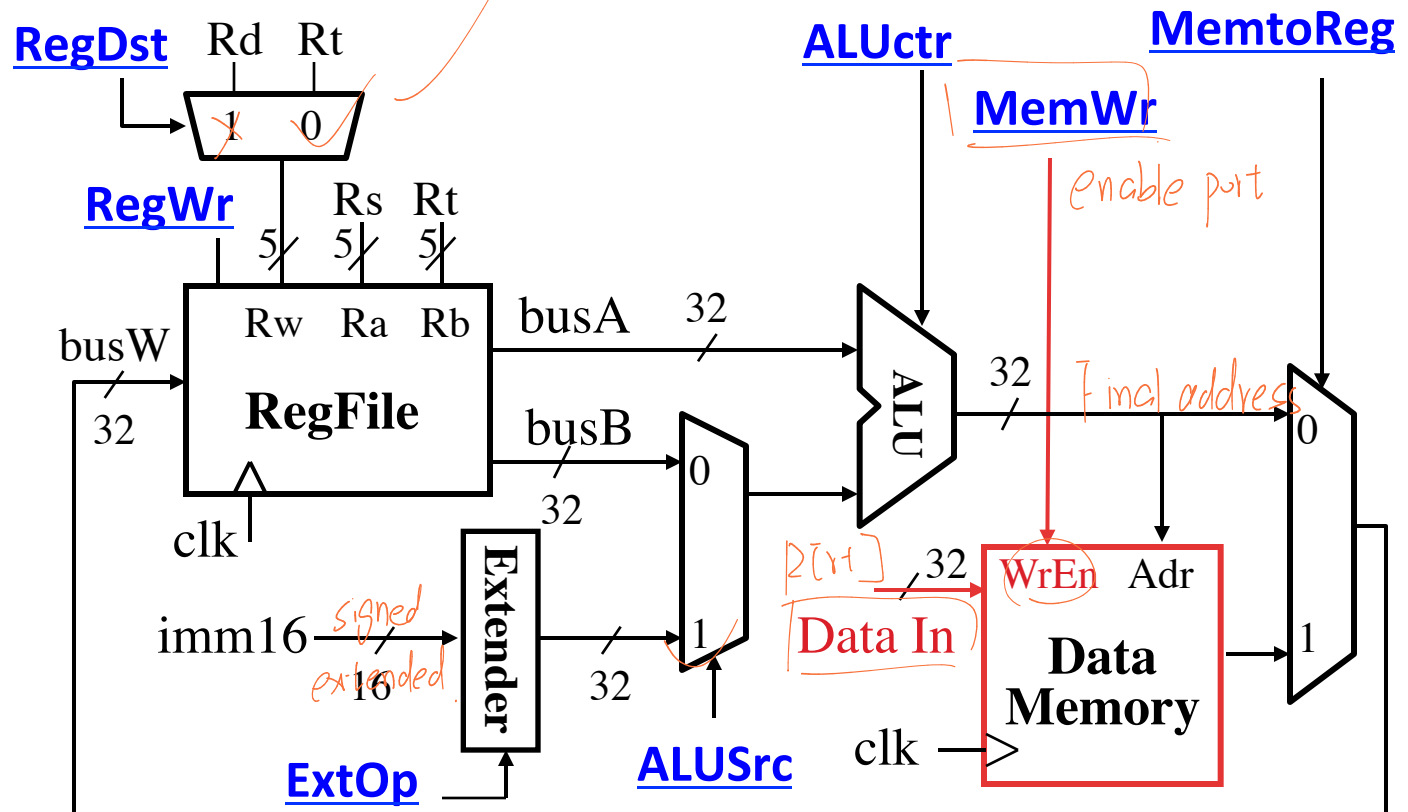 


3e: Store Operations

- Mem[R[rs] + SignExt[imm16]] = R[rt]

Ex.: sw rt, rs, imm16

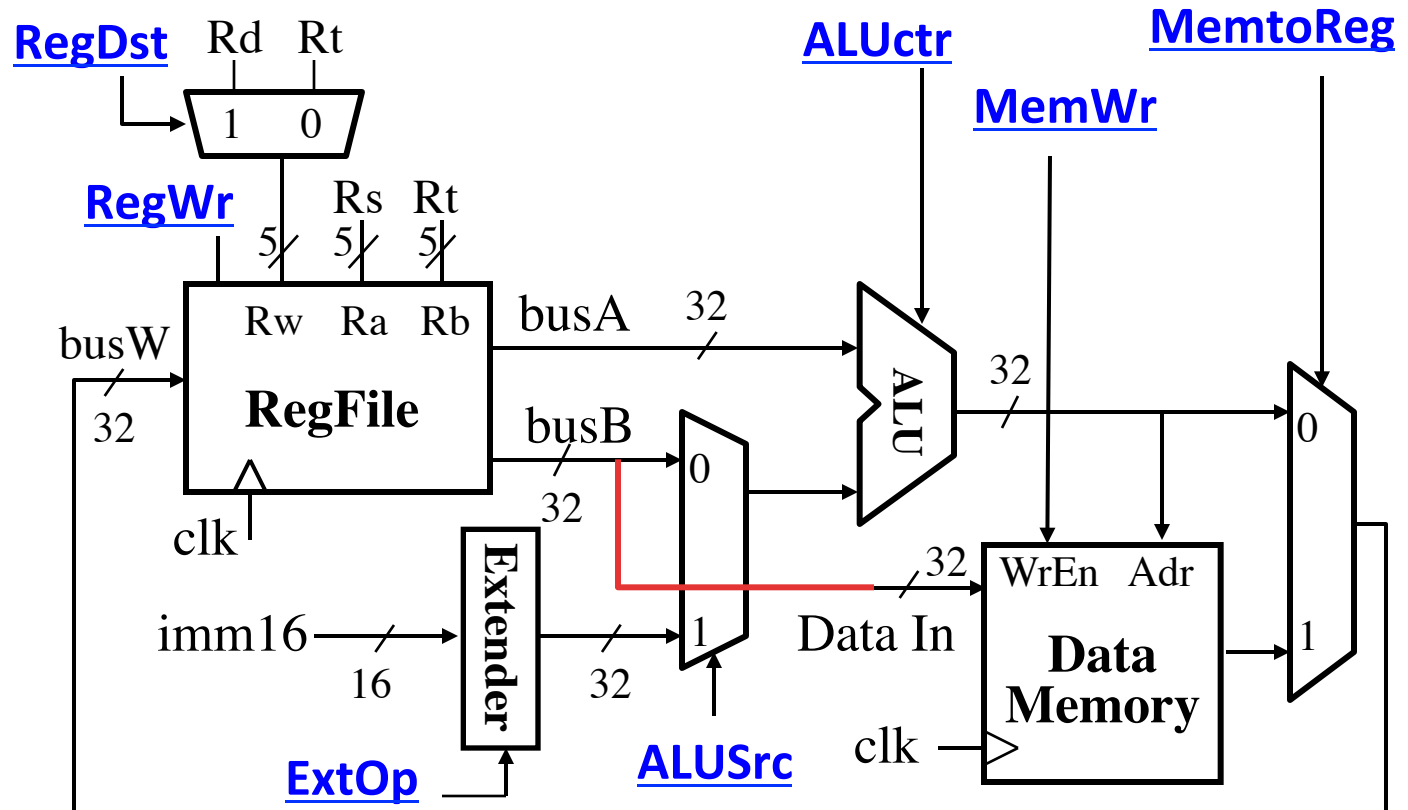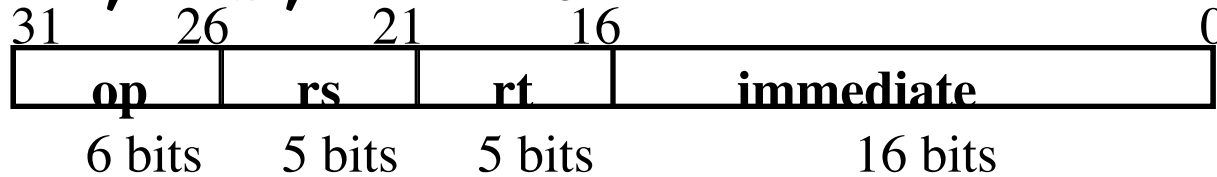

3f: The Branch Instruction

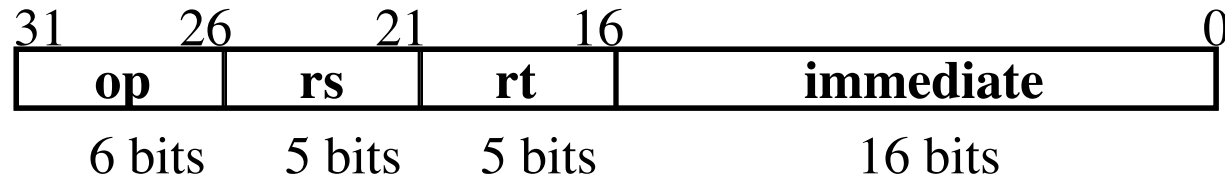


`beq rs, rt, imm16`

- `mem[PC]` Fetch the instruction from memory
- Equal = $(R[rs] == R[rt])$ Calculate branch condition
- if (Equal) Calculate the next instruction's address
 - $PC = PC + 4 + (\text{SignExt}(\text{imm16}) \times 4)$
- else
 - $PC = PC + 4$

Datapath for Branch Operations


beq rs, rt, imm16

 


6 bits 5 bits 5 bits 16 bits

Datapath generates condition (Equal)


Inst Address

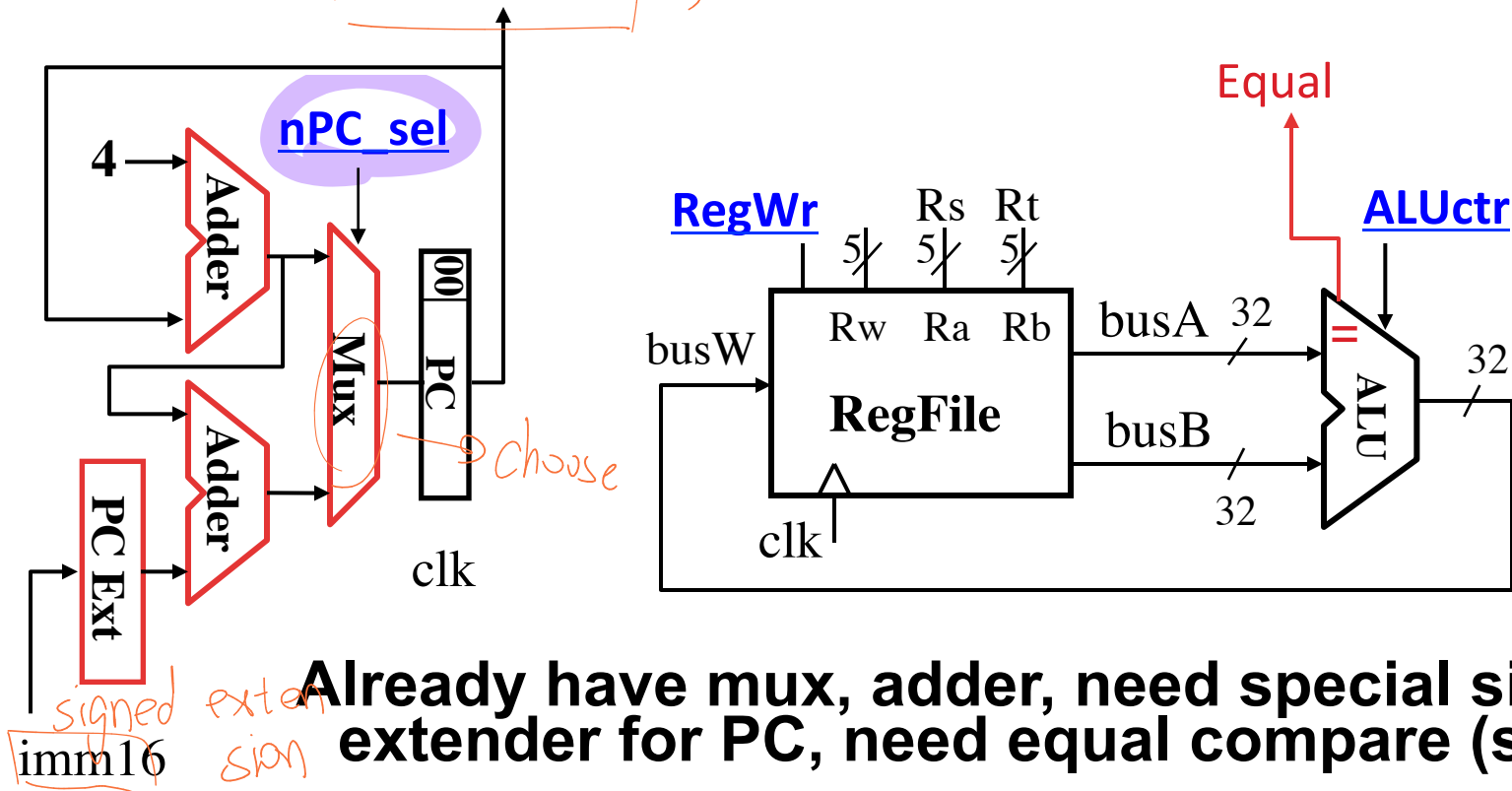

Instruction Fetch Unit including Branch

 

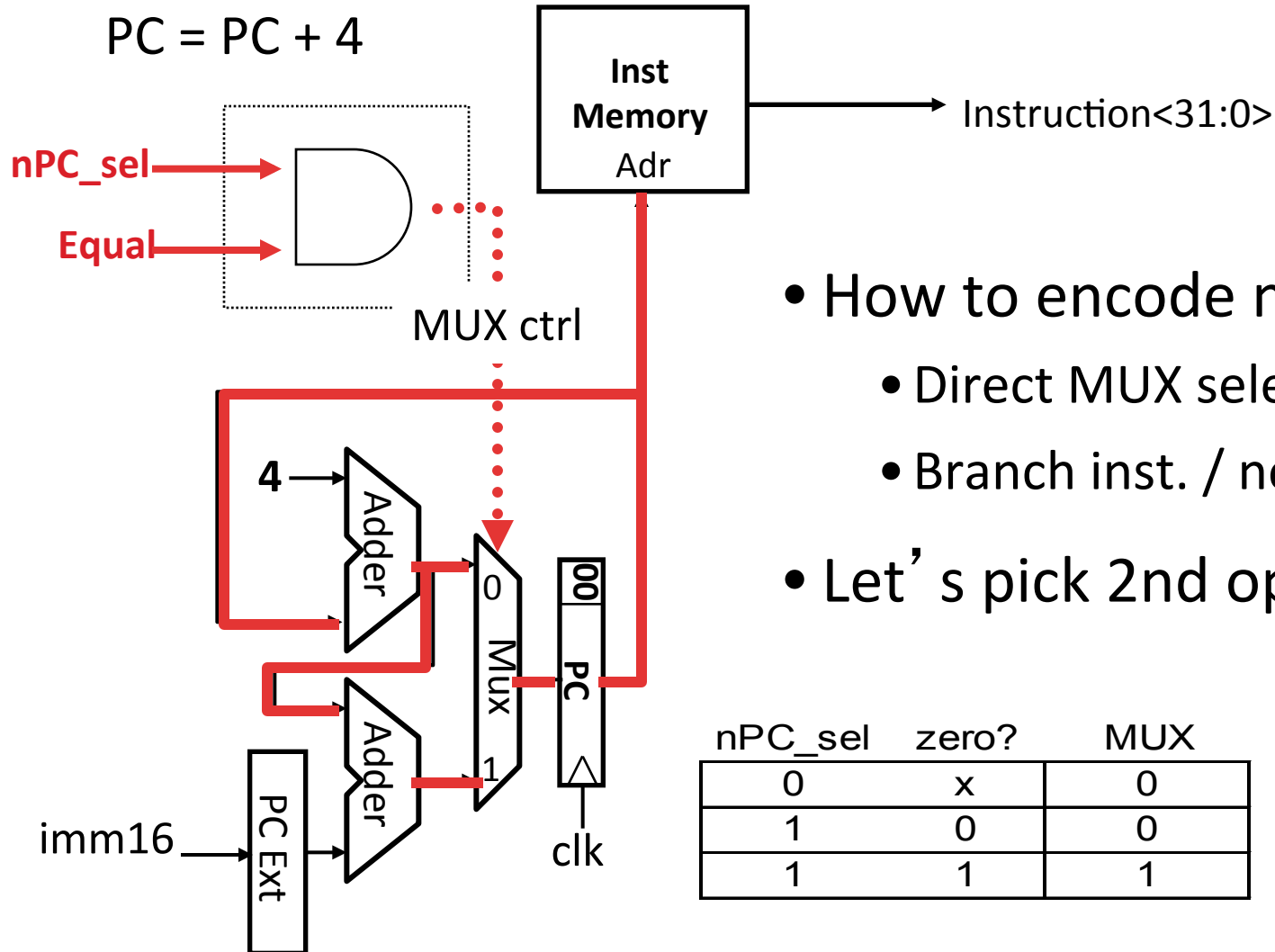- if (Zero == 1) then $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$; else $PC = PC + 4$




- How to encode nPC_sel?
 - Direct MUX select?
 - Branch inst. / not branch inst.
- Let's pick 2nd option

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1

Q: What logic gate?
And' Gate

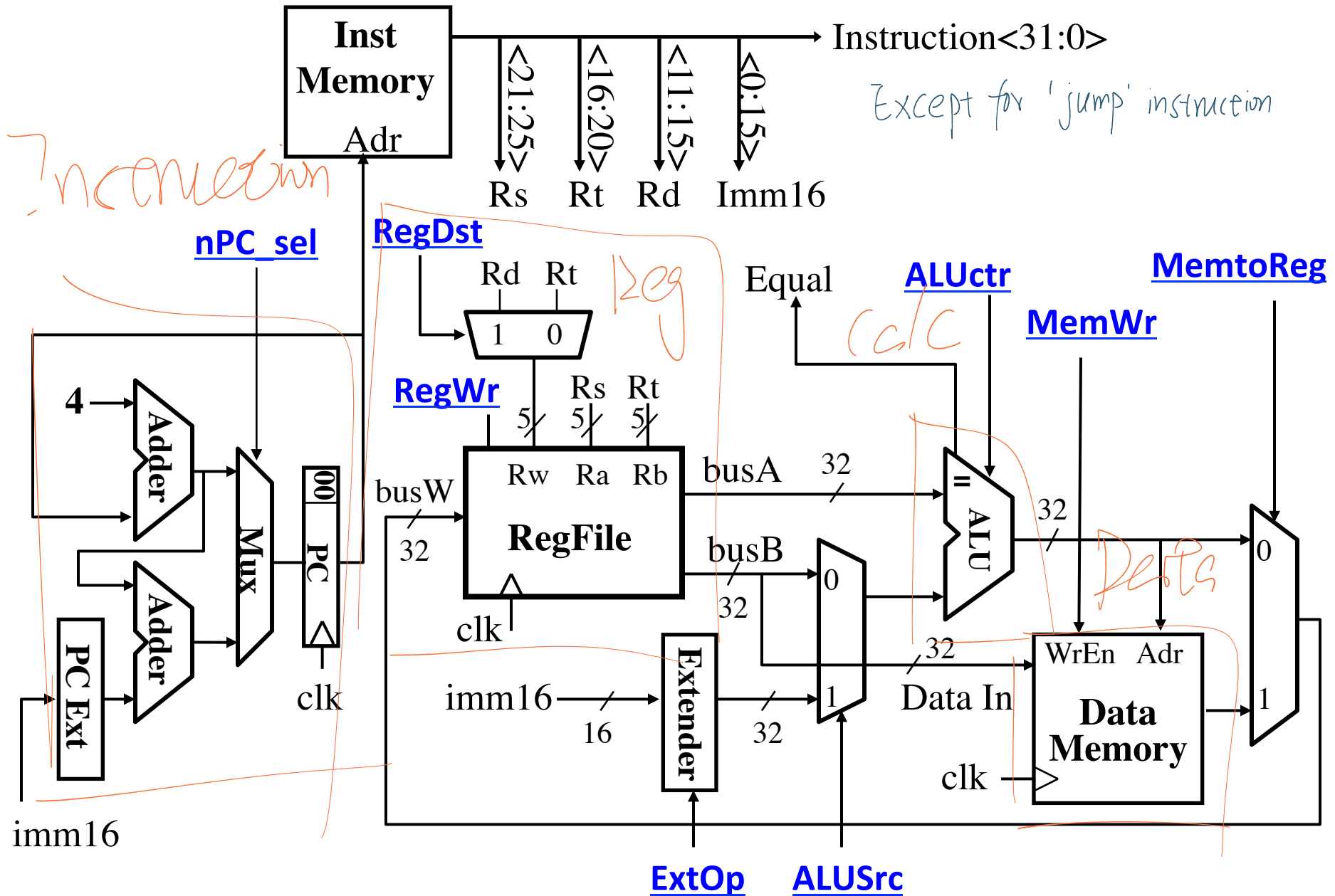Putting it All Together: A Single Cycle Datapath




Clickers/Peer Instruction

What new (pseudo)instruction would need no new datapath hardware?

- A: branch if reg==immediate.
- B: add two registers and branch if result zero
- C: store with auto-increment of base address:
 - sw rt, rs, offset // rs incremented by offset after store
- D: shift left logical by one bit

 Closest / ALU have the capability to finish comparison.



Administrivia


Datapath Control Signals

extension


- **ExtOp:** “zero”, “sign”
- **ALUSrc:** 0 \Rightarrow regB;
1 \Rightarrow imm
- **ALUctr:** “ADD”, “SUB”, “OR”

all of the instructions.

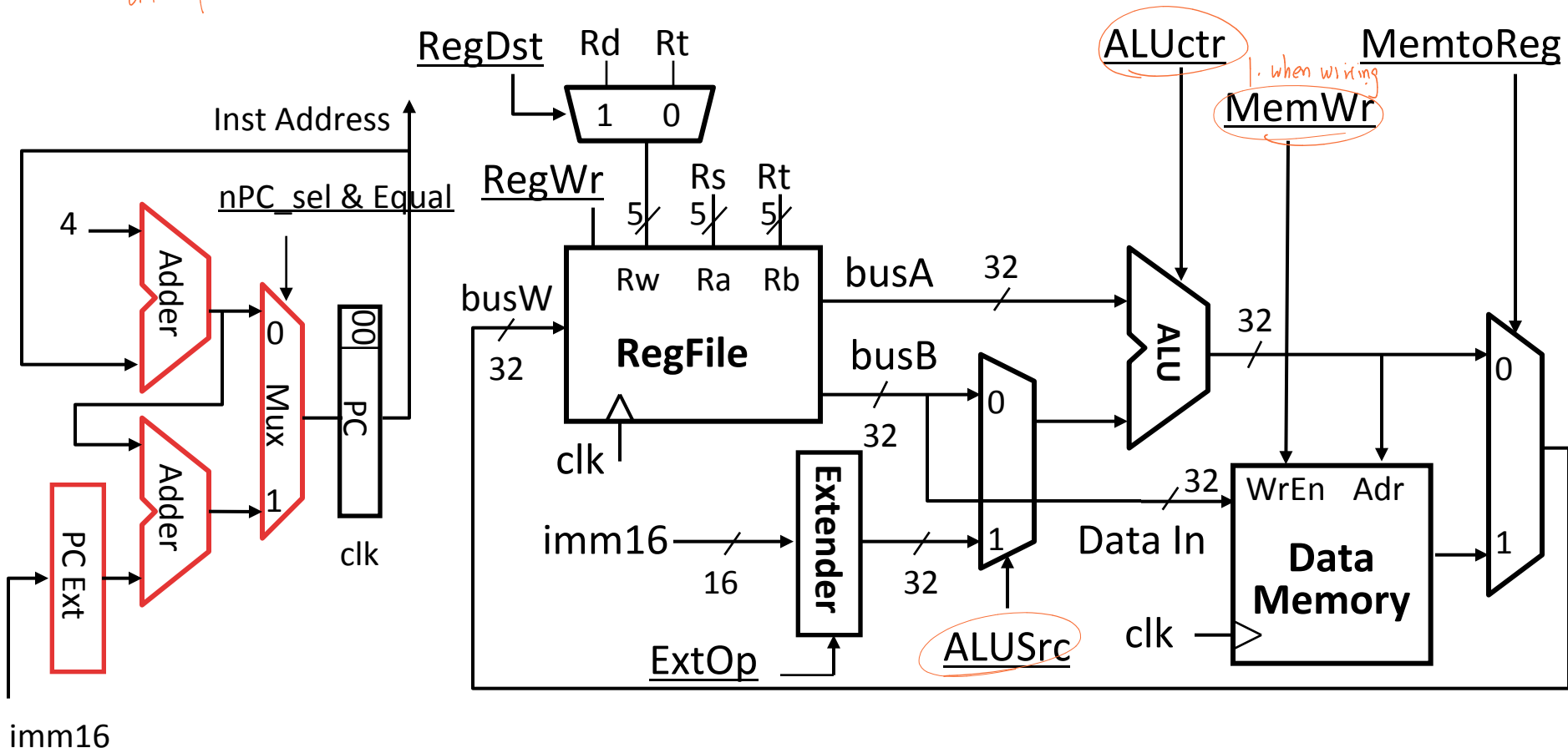
- **MemWr:** 1 \Rightarrow write memory
- **MemtoReg:** 0 \Rightarrow ALU; 1 \Rightarrow Mem
- **RegDst:** 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- **RegWr:** 1 \Rightarrow write register



Given Datapath: RTL \rightarrow Control

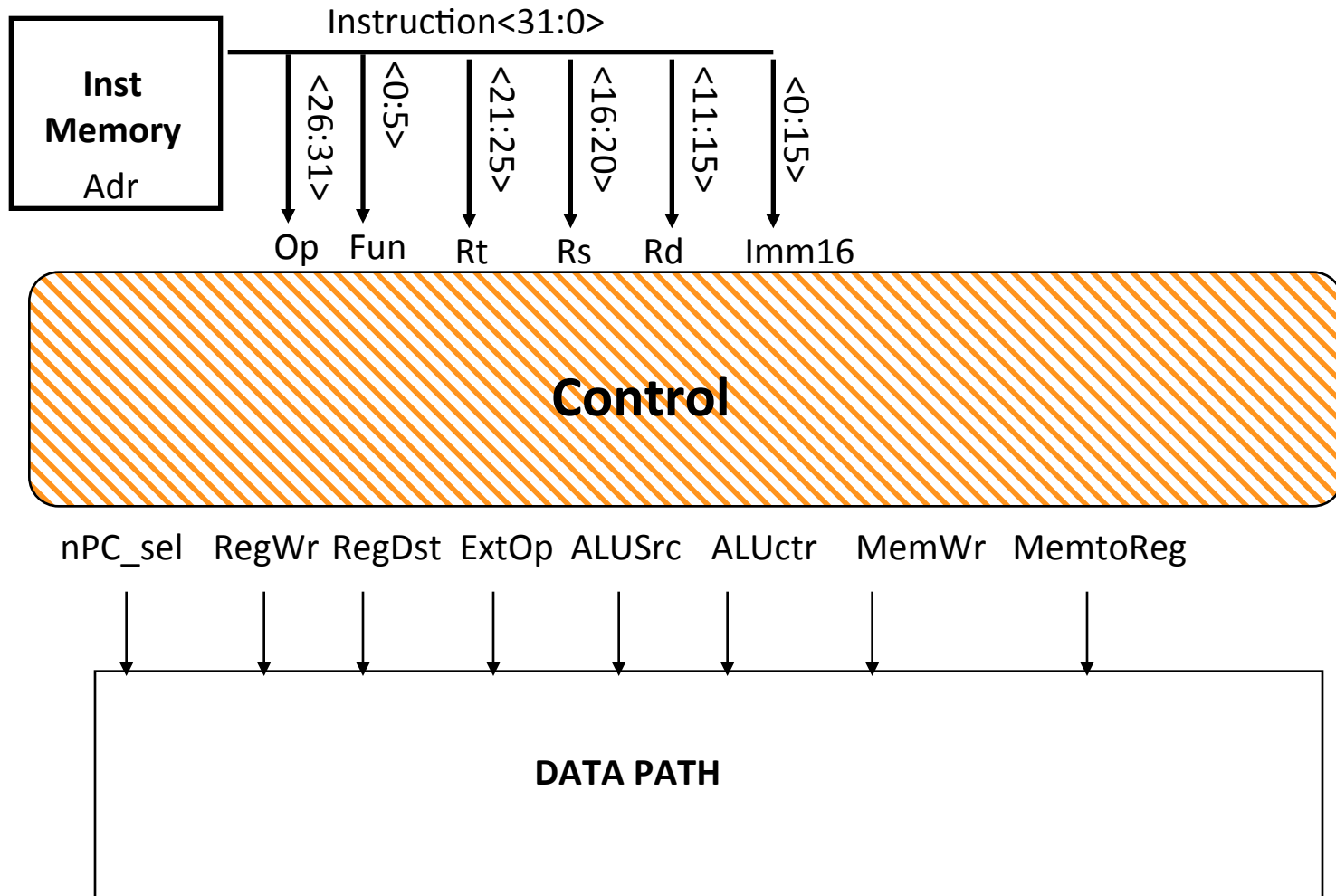

RTL: The Add Instruction

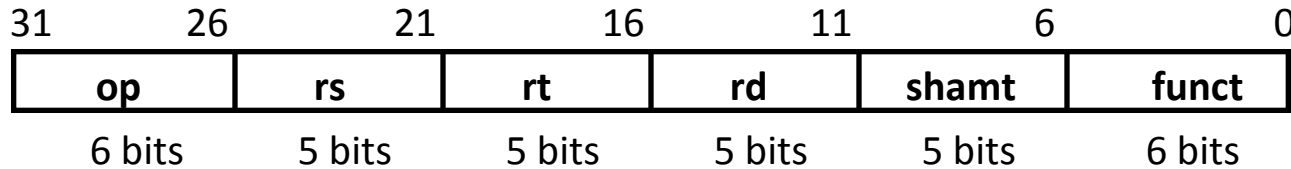

add rd, rs, rt


- MEM[PC] Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$ The actual operation
- $PC = PC + 4$ Calculate the next instruction's address

Instruction Fetch Unit at the Beginning of Add


- Fetch the instruction from Instruction

memory: $\text{Instruction} = \text{MEM}[\text{PC}]$

- same for all instructions

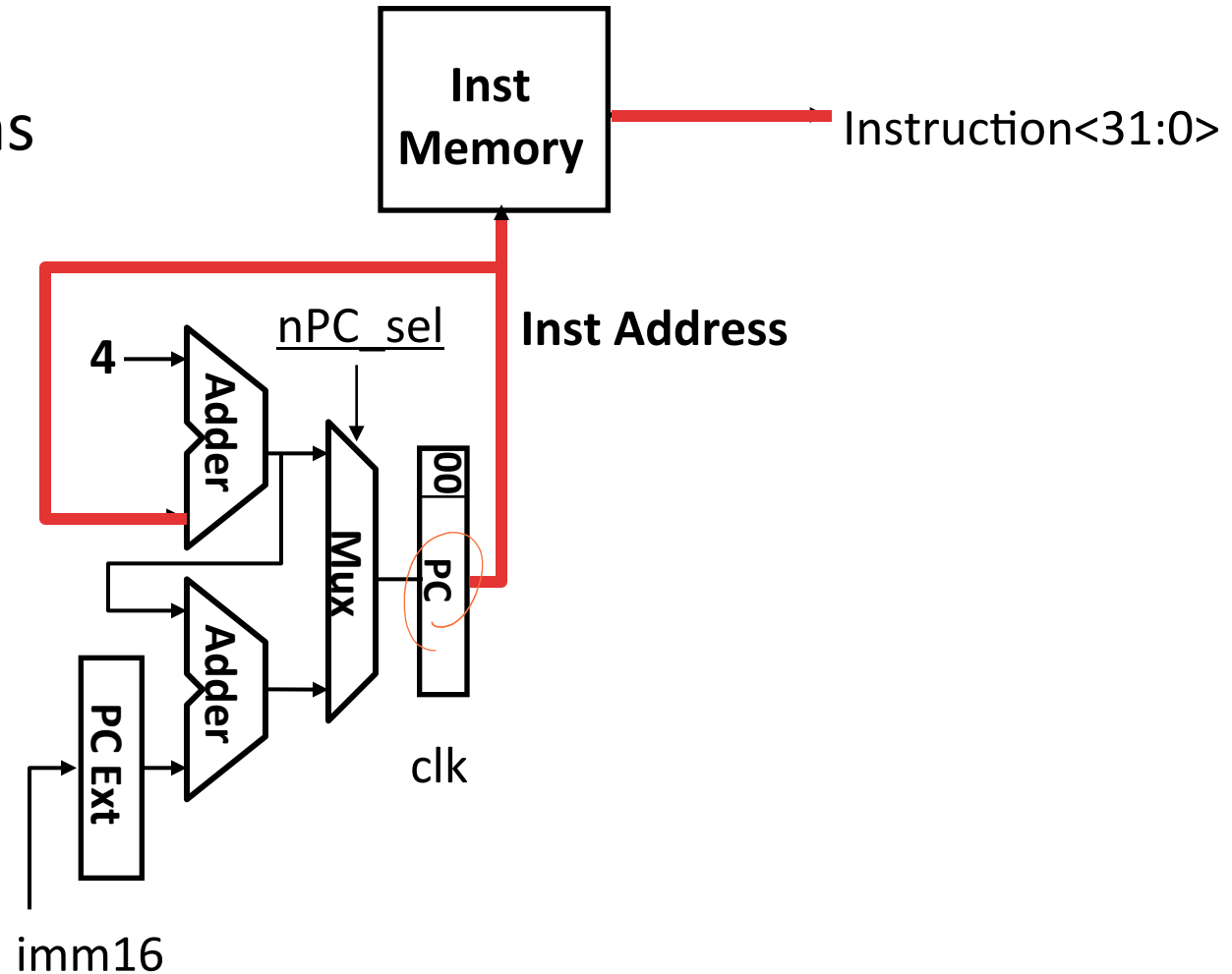


Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

Write into the register

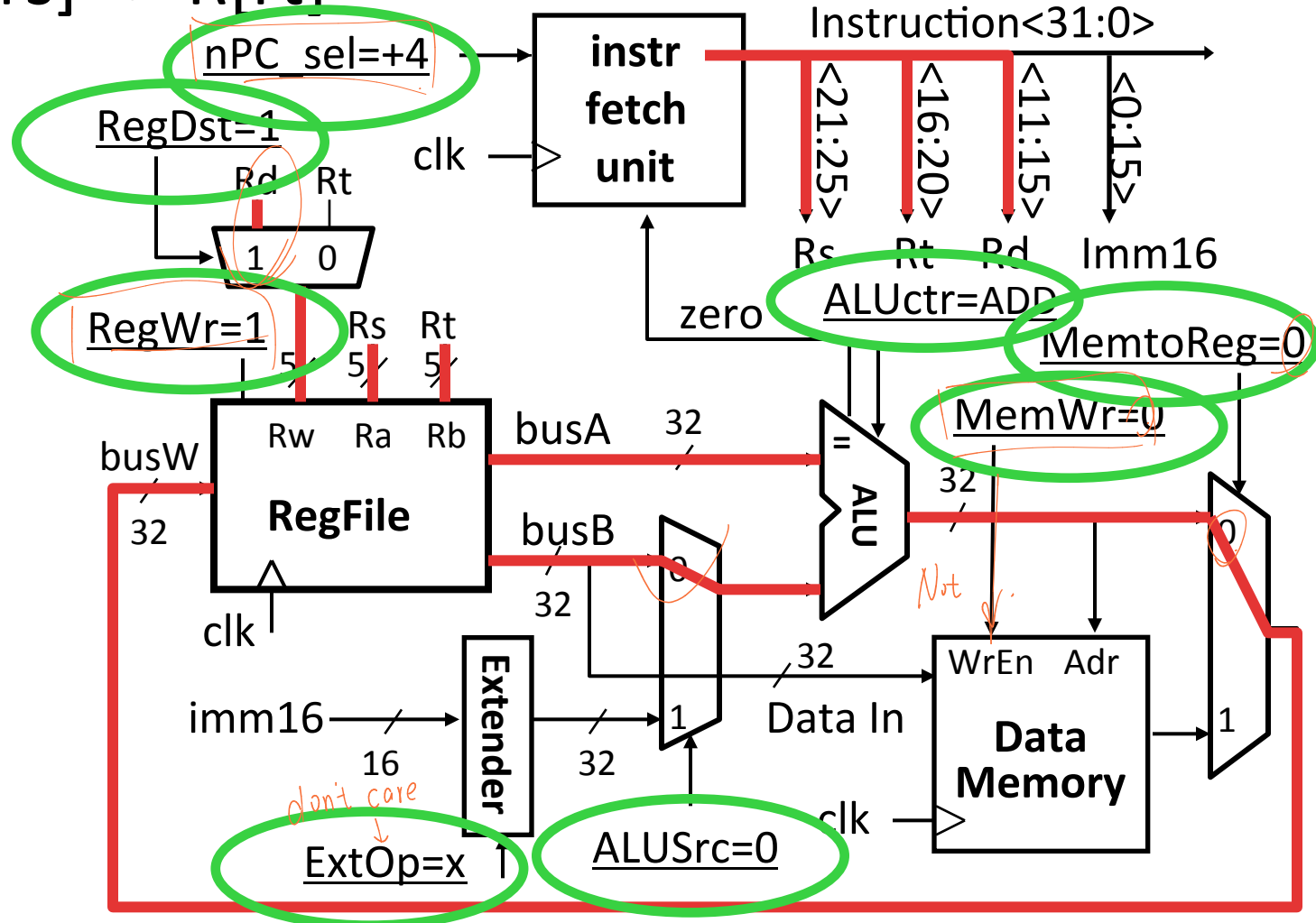

Instruction Fetch Unit at End of Add

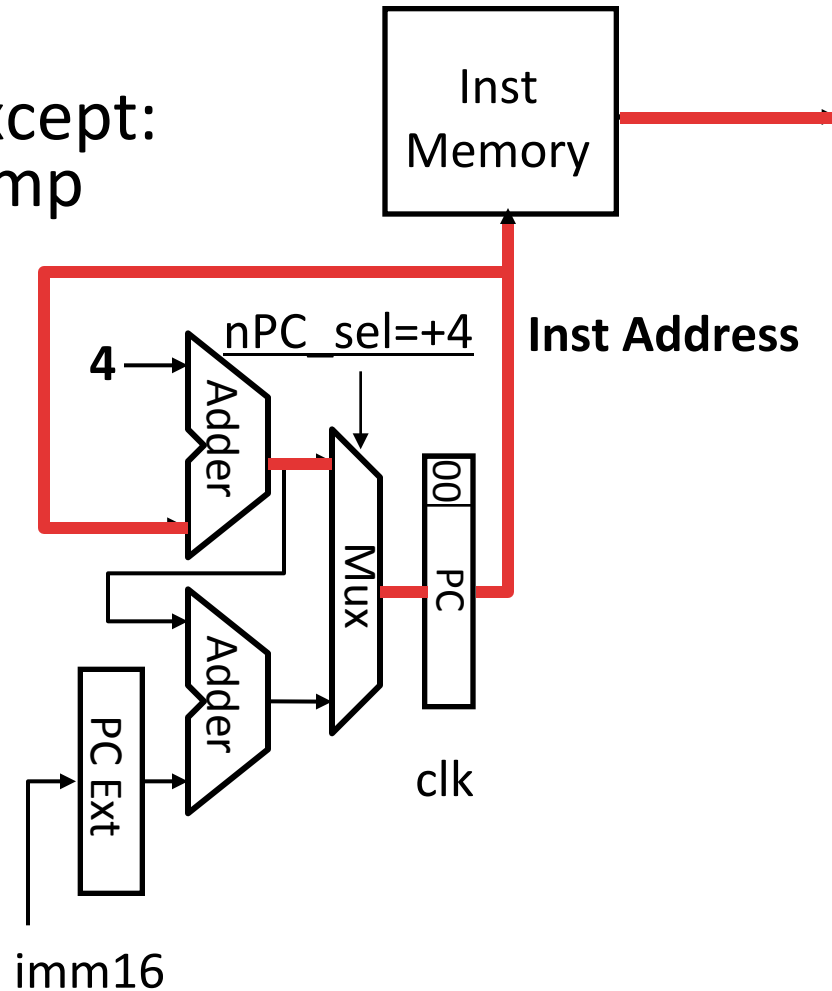
- $PC = PC + 4$
 - Same for all instructions except: Branch and Jump



Single Cycle Datapath during Jump



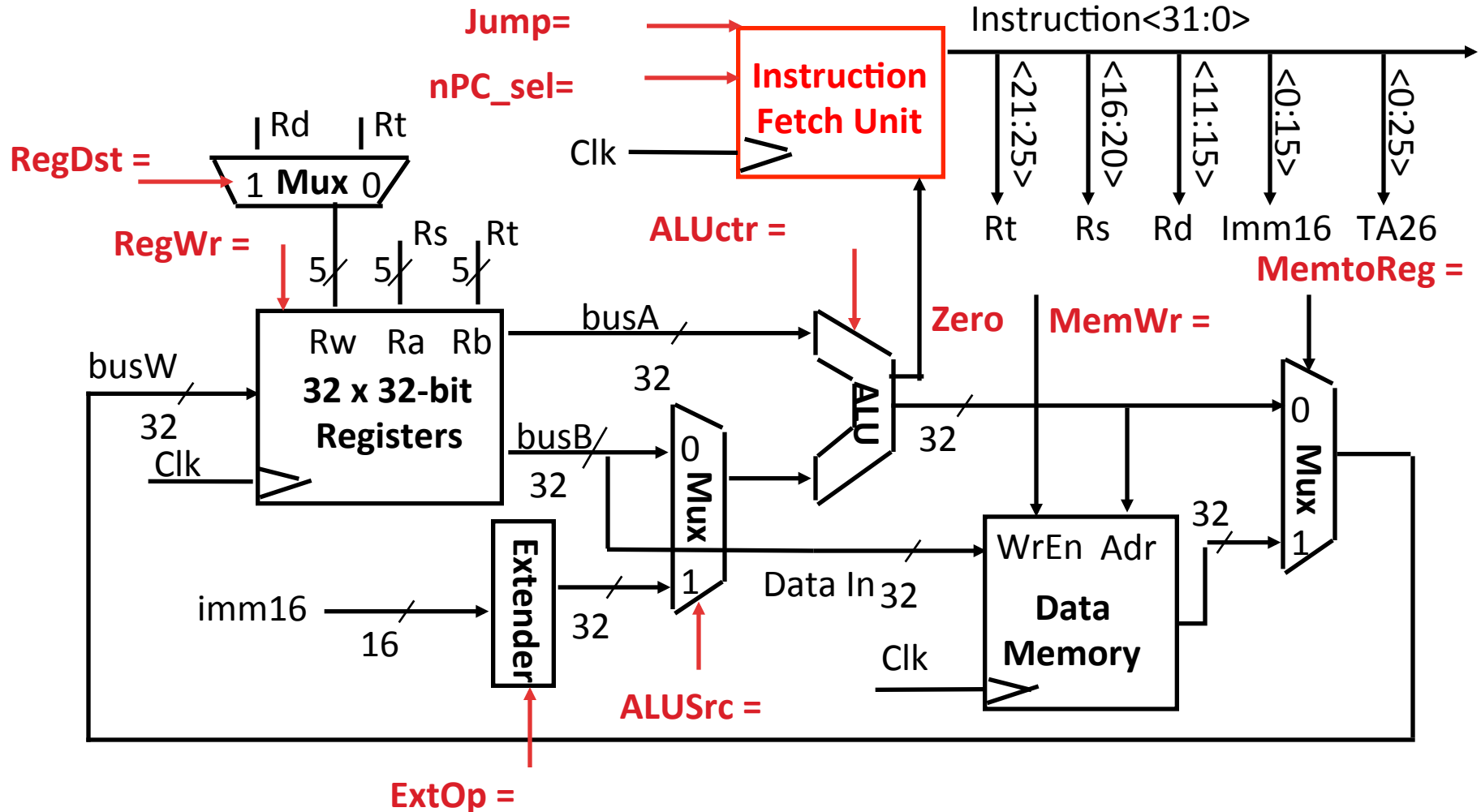
- New PC = { PC[31..28], target address, 00 }



Single Cycle Datapath during Jump



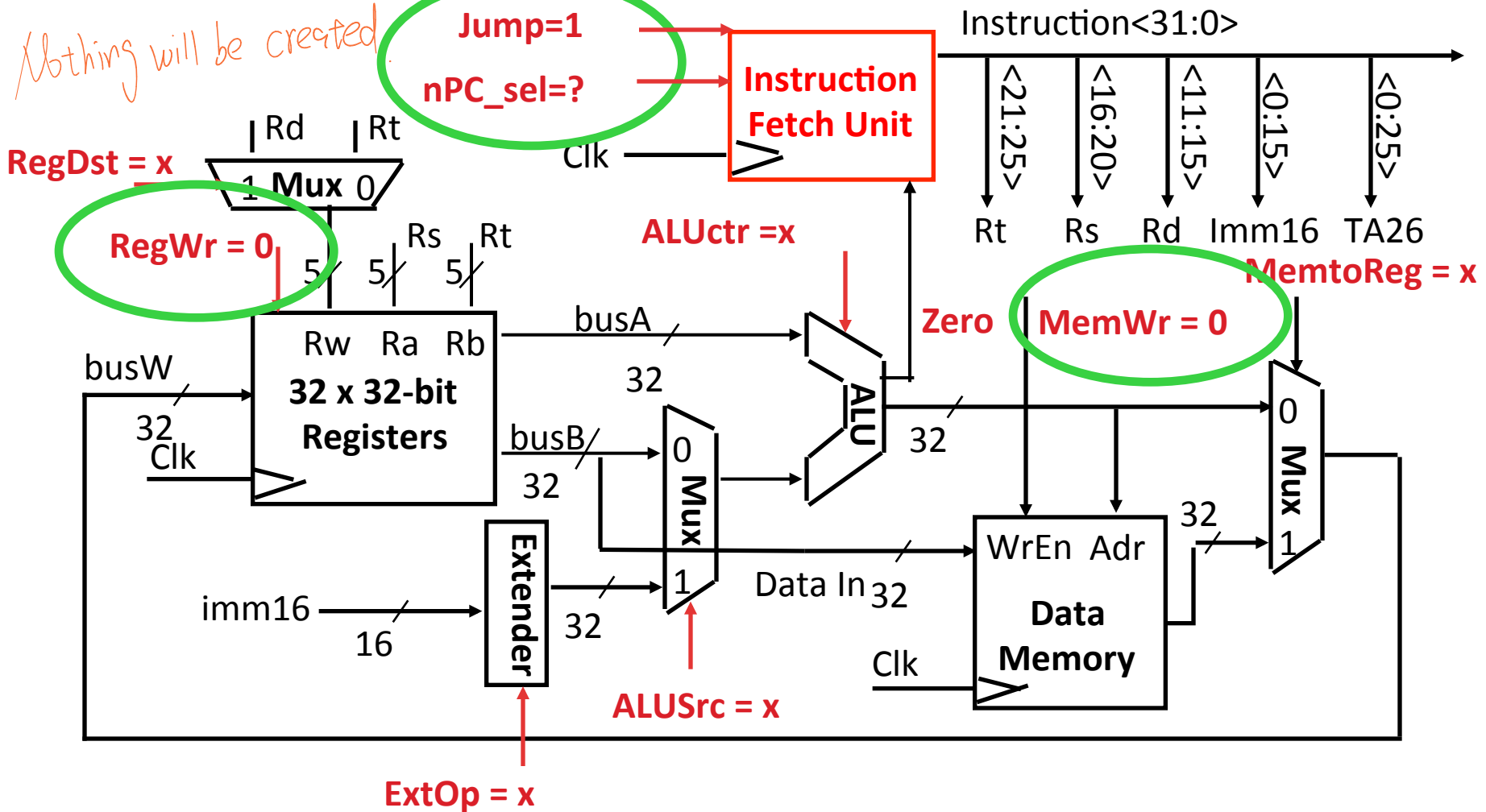
- New PC = { PC[31..28], target address, 00 }



Instruction Fetch Unit at the End of Jump



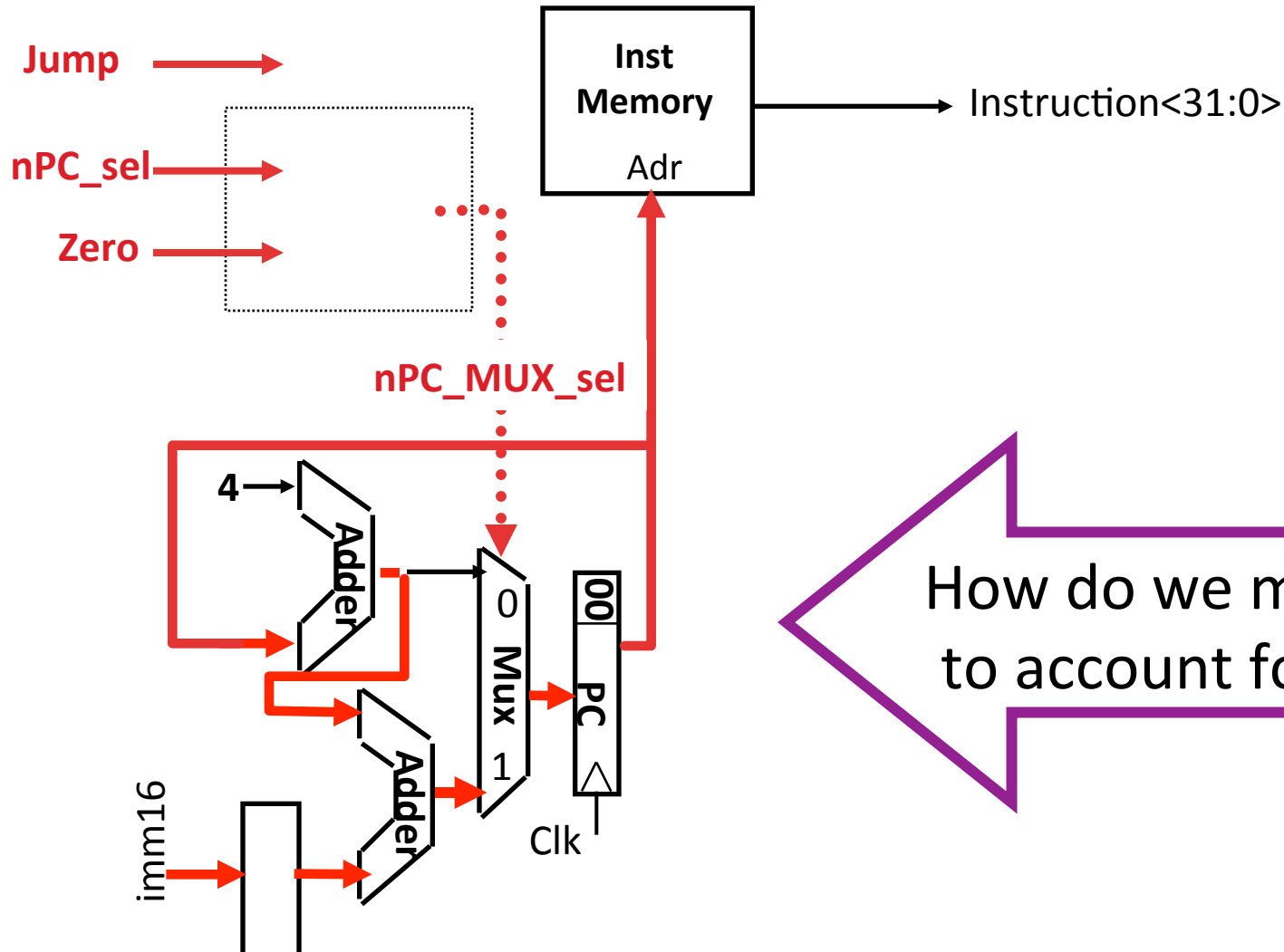- New PC = { PC[31..28], target address, 00 }




How do we modify this to account for jumps?

Instruction Fetch Unit at the End of Jump



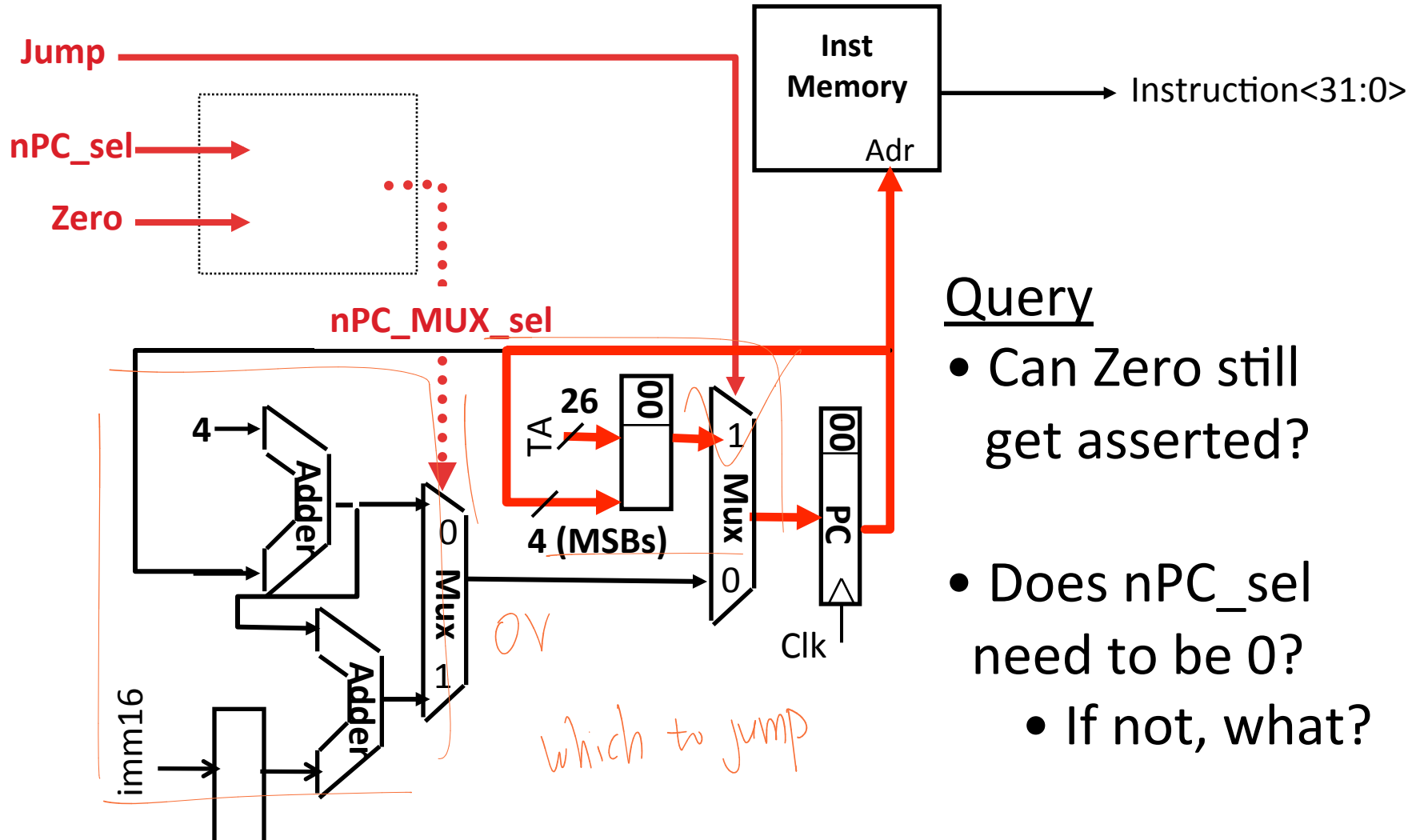- New PC = { PC[31..28], target address, 00 }




Query

- Can Zero still get asserted?
- Does nPC_sel need to be 0?
 - If not, what?

In The News: Tile-Mx100

100 64-bit ARM cores on one chip

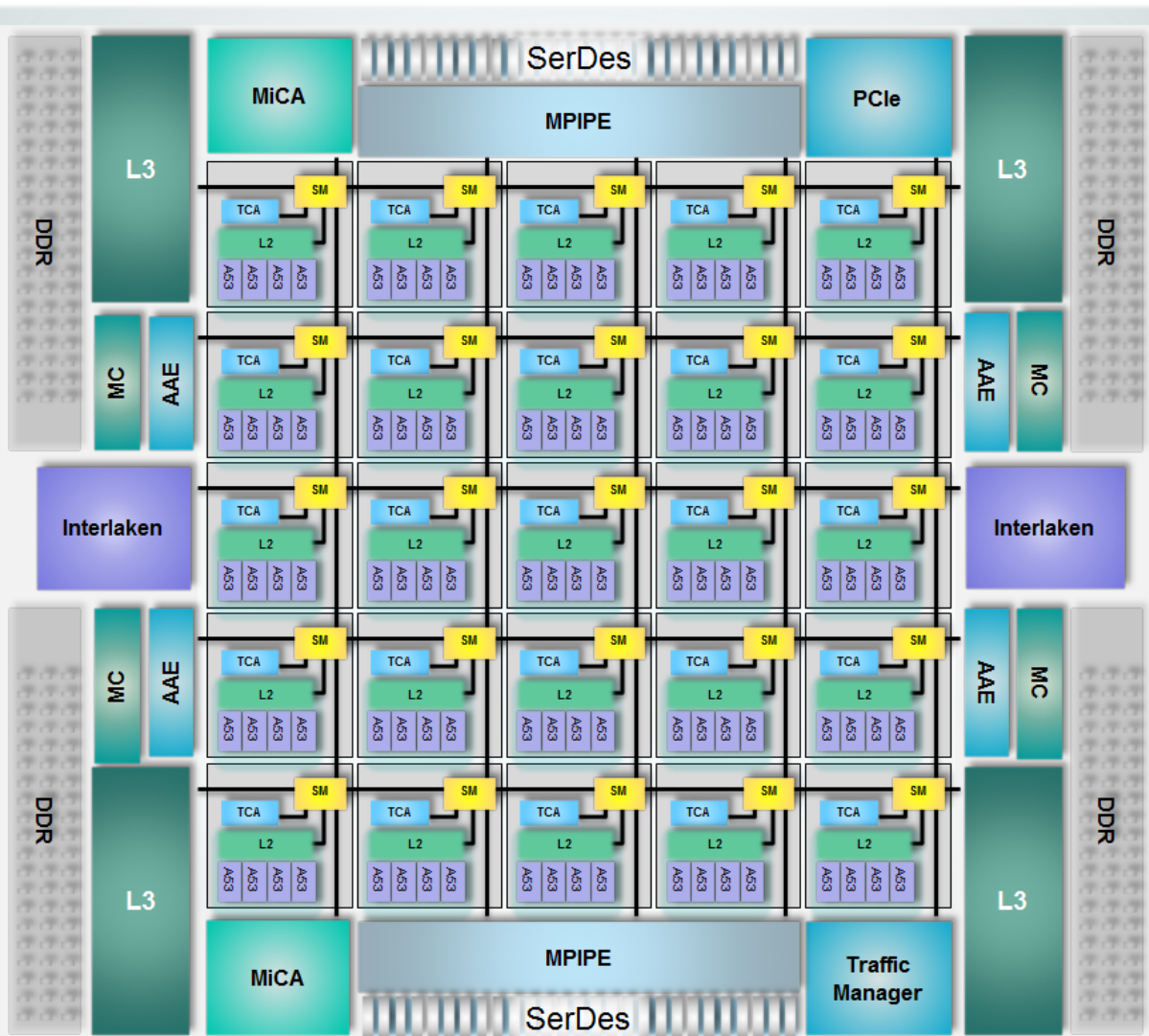


EZChip (bought Tiler)

100 64-bit ARM Cortex A53

- Dual-issue, in-order

P&H Figure 4.17

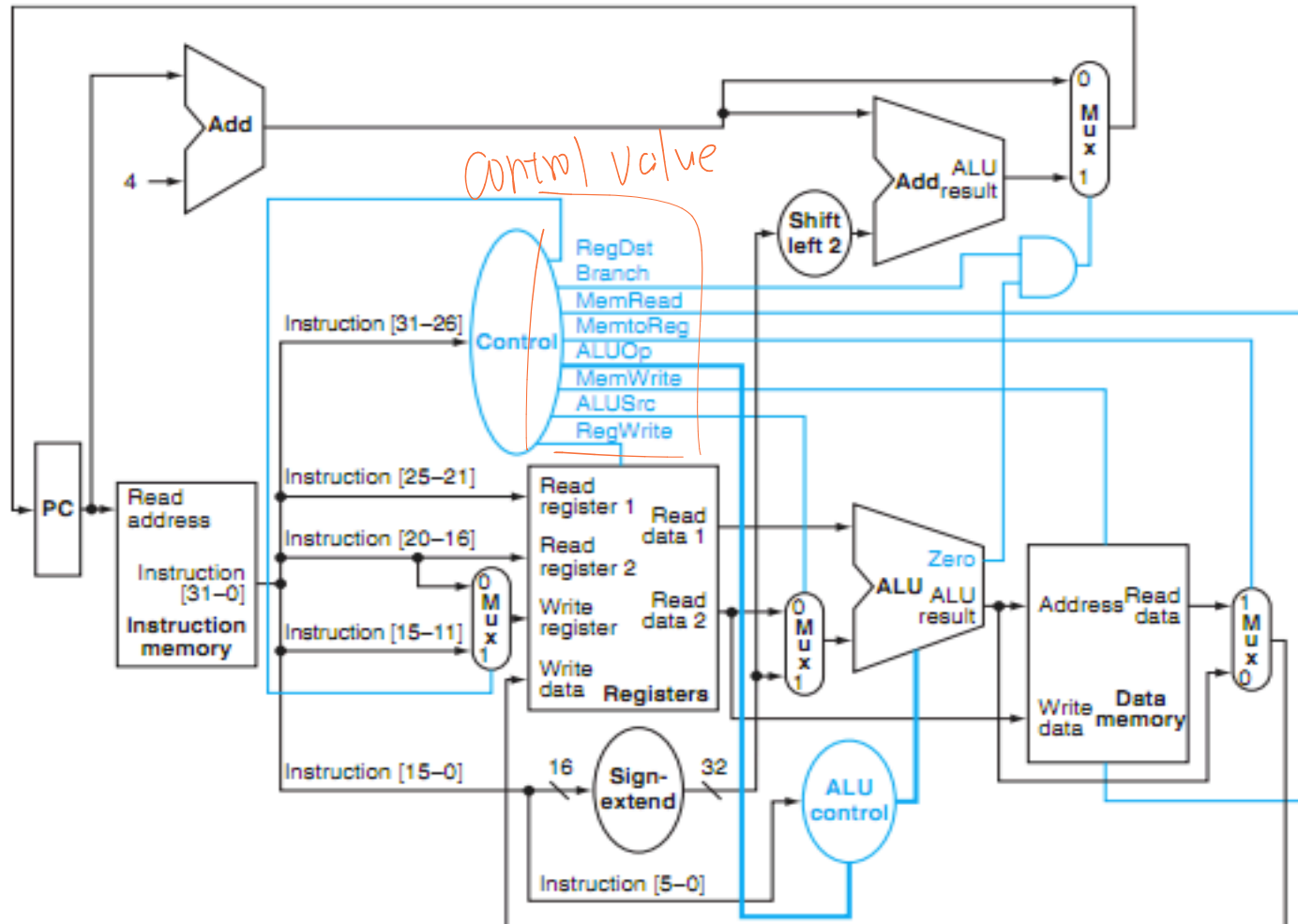

Summary of the Control Signals (1/2)

inst Register Transfer

add $R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$

ALUSrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"

sub $R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4$

ALUSrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"

ori $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16}); PC \leftarrow PC + 4$

ALUSrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"

lw $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})]; PC \leftarrow PC + 4$

ALUSrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,
nPC_sel = "+4"

sw $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs]; PC \leftarrow PC + 4$

ALUSrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"

beq if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(\text{Imm16})$ || 00
else $PC \leftarrow PC + 4$

nPC_sel = "br", ALUctr = "SUB"

Summary of the Control Signals (2/2)

Truth table

See Appendix A

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

	31	26	21	16	11	6	0	
R-type	op	rs	rt	rd	shamt	funct		add, sub
I-type	op	rs	rt	immediate				ori, lw, sw, beq
J-type	op	target address						jump



Boolean Expressions for Controller

```
RegDst      = add + sub
ALUSrc      = ori + lw + sw
MemtoReg    = lw
RegWrite    = add + sub + ori + lw
MemWrite    = sw
nPCsel      = beq
Jump        = jump
ExtOp       = lw + sw
ALUctr[0]   = sub + beq    (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1]   = or
```


Where:

```
rtype = ~op5 • ~op4 • ~op3 • ~op2 • ~op1 • ~op0,
ori    = ~op5 • ~op4 • op3 • op2 • ~op1 • op0
lw     = op5 • ~op4 • ~op3 • ~op2 • op1 • op0
sw     = op5 • ~op4 • op3 • ~op2 • op1 • op0
beq    = ~op5 • ~op4 • ~op3 • op2 • ~op1 • ~op0
jump   = ~op5 • ~op4 • ~op3 • ~op2 • op1 • ~op0
```

```
add = rtype • func5 • ~func4 • ~func3 • ~func2 • ~func1 • ~func0
sub = rtype • func5 • ~func4 • ~func3 • ~func2 • func1 • ~func0
```

How do we
implement this in
gates?

Controller Implementation

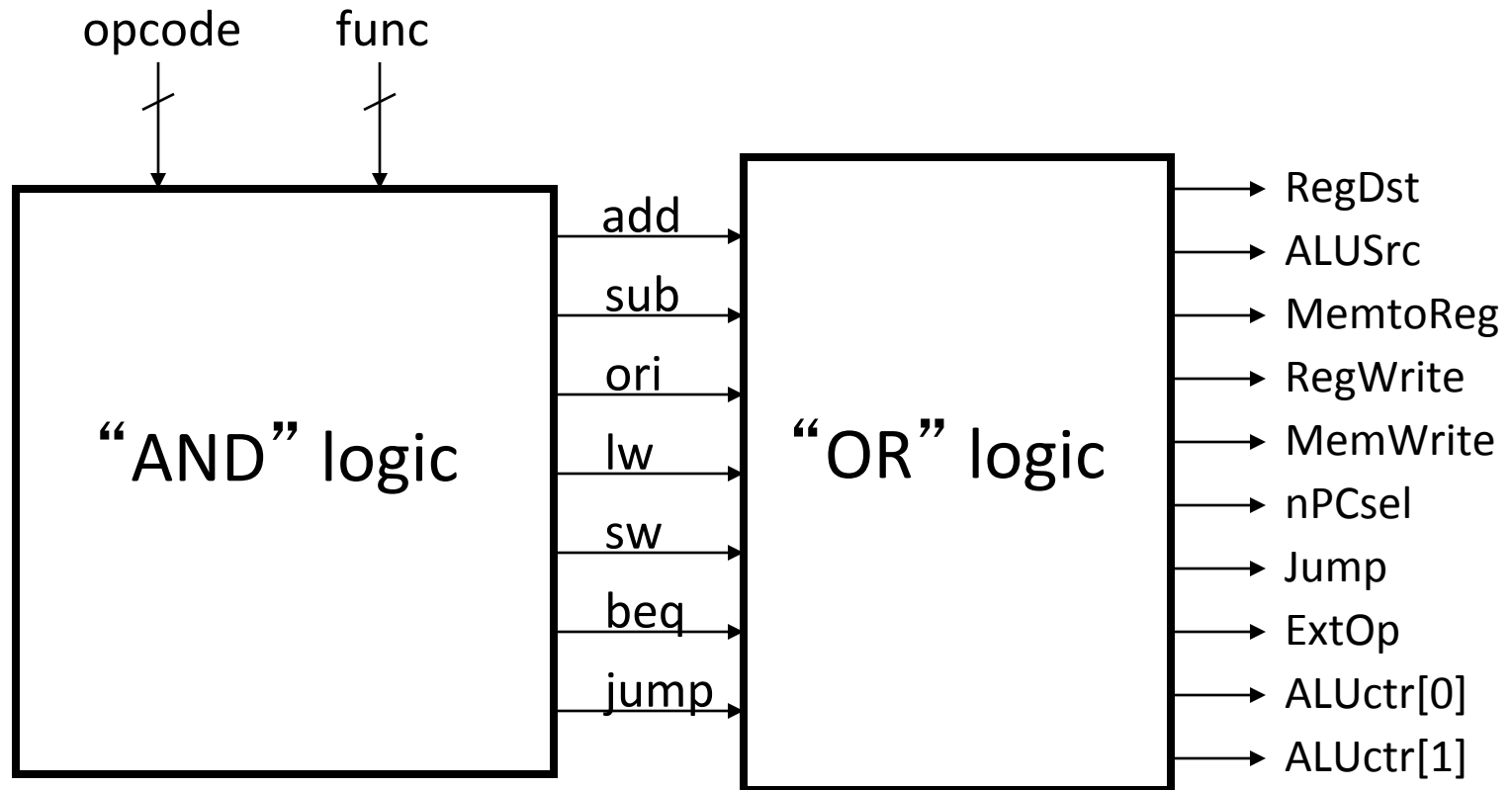

Summary: Single-cycle Processor

- Five steps to design a processor:

1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits

